

# Computational Microelectronics

## Lecture 22 Transient

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# RC Circuit

# Euler schemes (Copied from L4)

- Forward Euler scheme

- In the forward Euler scheme, the time derivative is calculated by taking the difference between the **future** and **present** values:

$$\left. \frac{\partial C(x_i)}{\partial t} \right|_{t_k} \approx \frac{C(t_{k+1}) - C(t_k)}{t_{k+1} - t_k}$$

- Backward Euler scheme


- In the backward Euler scheme, the time derivative is calculated by taking the difference between the **present** and **past** values:

$$\left. \frac{\partial C(x_i)}{\partial t} \right|_{t_k} \approx \frac{C(t_k) - C(t_{k-1})}{t_k - t_{k-1}}$$
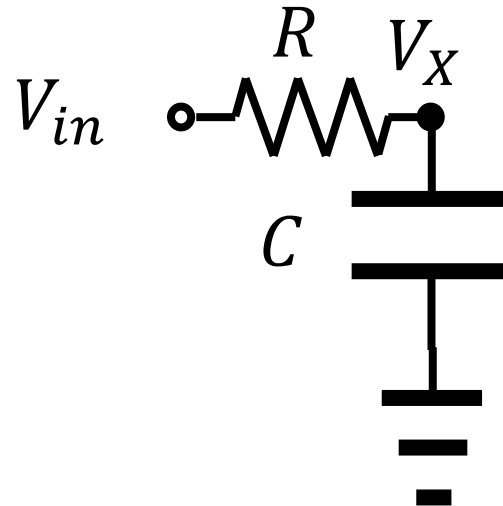
# RC circuit

- Consider a series RC circuit.
  - It is driven by a voltage source,  $V_{in}(t)$ . For  $t < 0$ , it was zero.

$$\frac{V_X - V_{in}(t)}{R} + C \frac{dV_X}{dt} = 0$$



# Analytic solution

- First-order differential equation

– At  $t = 0$ ,  $V_{in}(t)$  is suddenly ramped up to  $V_{DD}$ ,

$$V_X(t) = V_{DD} \left[ 1 - \exp\left(-\frac{t}{RC}\right) \right]$$

# Backward Euler

- Let us assume a constant time step,  $\Delta t$ .
  - At  $t_i = i\Delta t$  ( $i \geq 1$ ), the KCL can be discretized as

$$\frac{V_X(t_i) - V_{in}(t_i)}{R} + C \frac{V_X(t_i) - V_X(t_{i-1})}{\Delta t} = 0$$

- After a simple manipulation,

$$\left(1 + \frac{\Delta t}{RC}\right) V_X(t_i) = V_X(t_{i-1}) + \frac{\Delta t}{RC} V_{in}(t_i)$$

- For our present example,  $V_{in}(t_i)$  is always  $V_{DD}$ .

# Impact of Time Step

# **$R = C = V_{DD} = 1$ with their own dimensions**

- It means that  $R$  is 1  $\Omega$ ,  $C$  is 1 F, and  $V_{DD}$  is 1 V.

- In this case, the equation is simply written as

$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t$$



- Its analytic solution is

$$V_X(t_i) = 1 - \exp(-t_i)$$



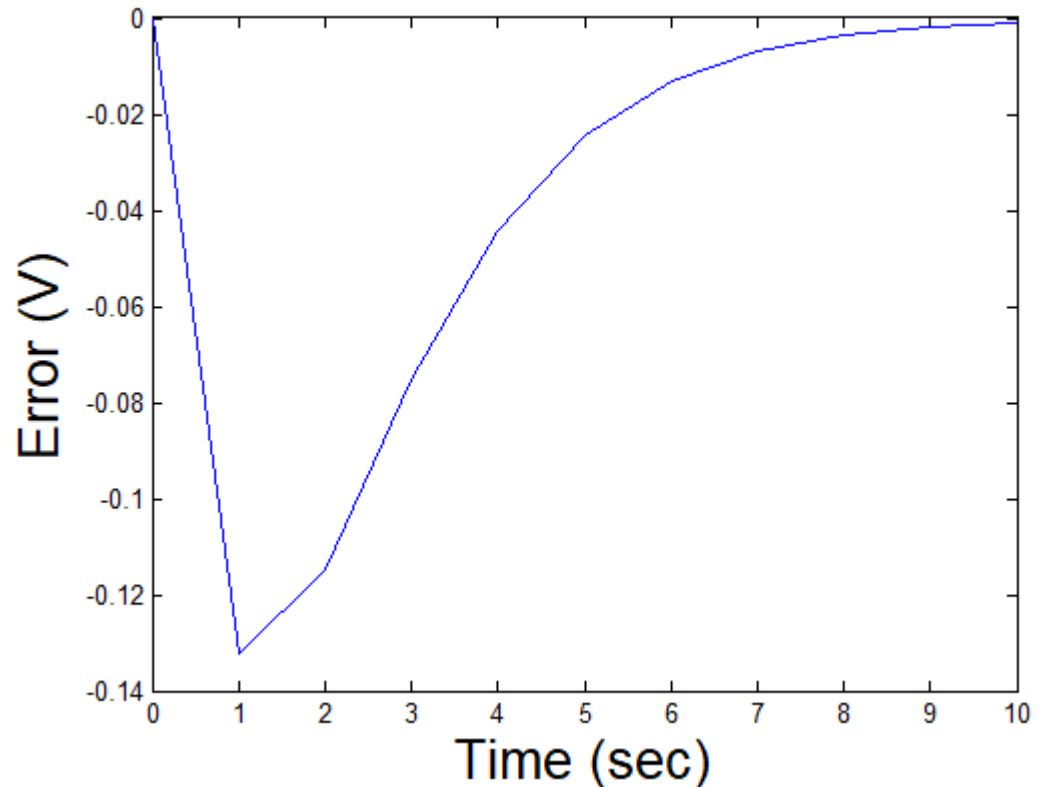
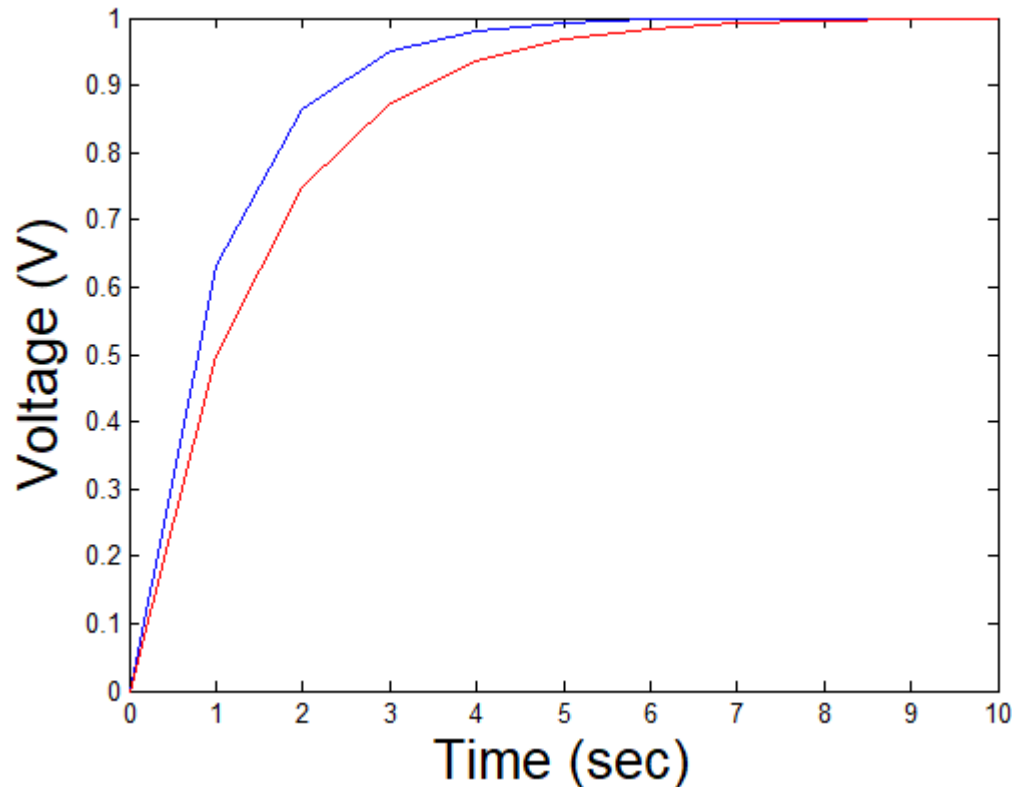
# Case study) $\Delta t = 1$

- Run the simulation up to 10 sec.
  - Exact solution (blue curve in left figure), numerical solution (red curve in left figure), and error (right figure)



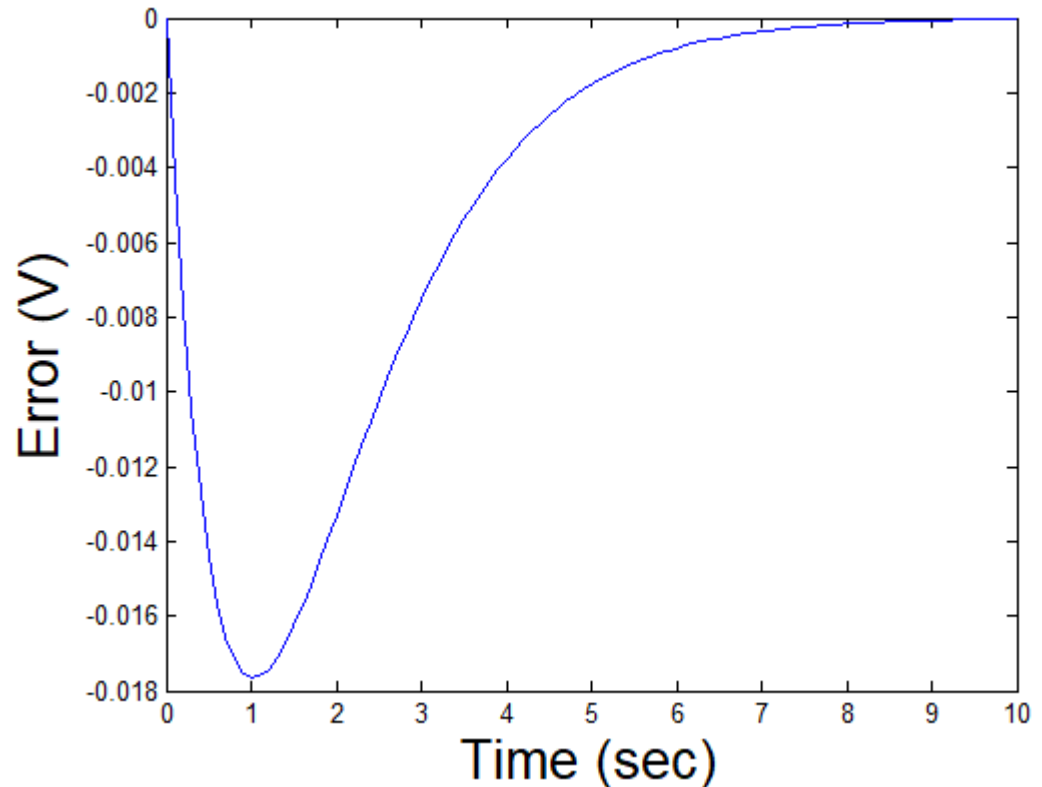
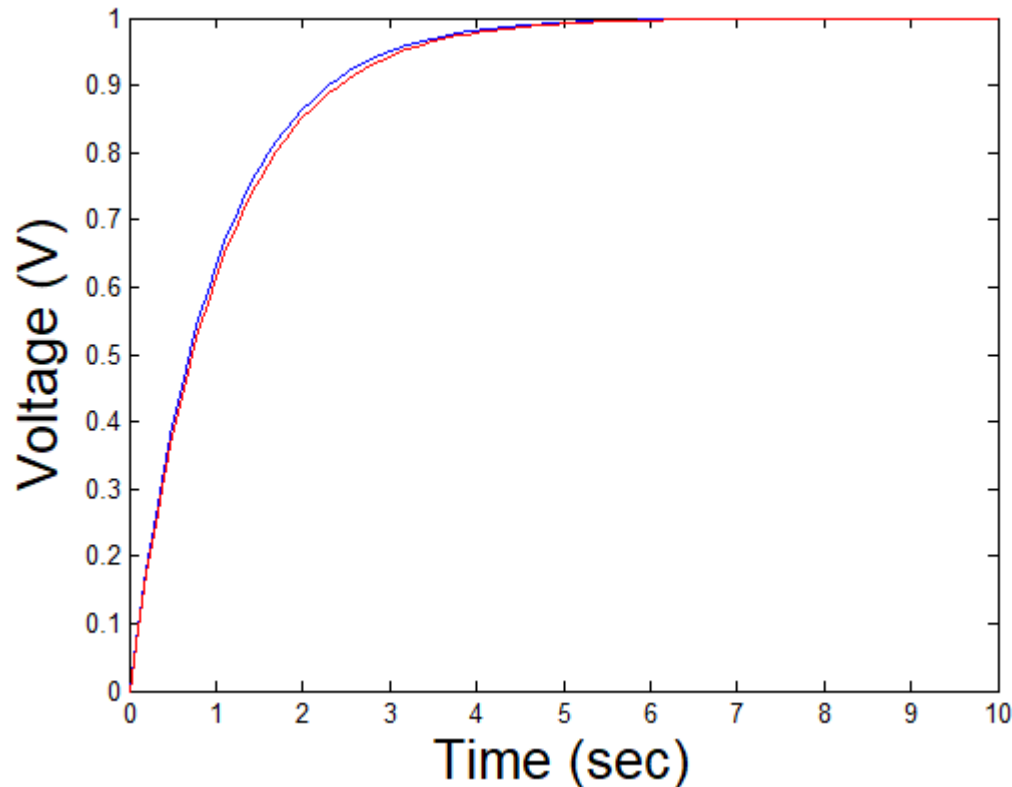
# Case study) $\Delta t = 0.1$

- Ten times shorter time spacing
  - It looks much better.
  - Still, we have the maximum difference larger than 0.01 V.


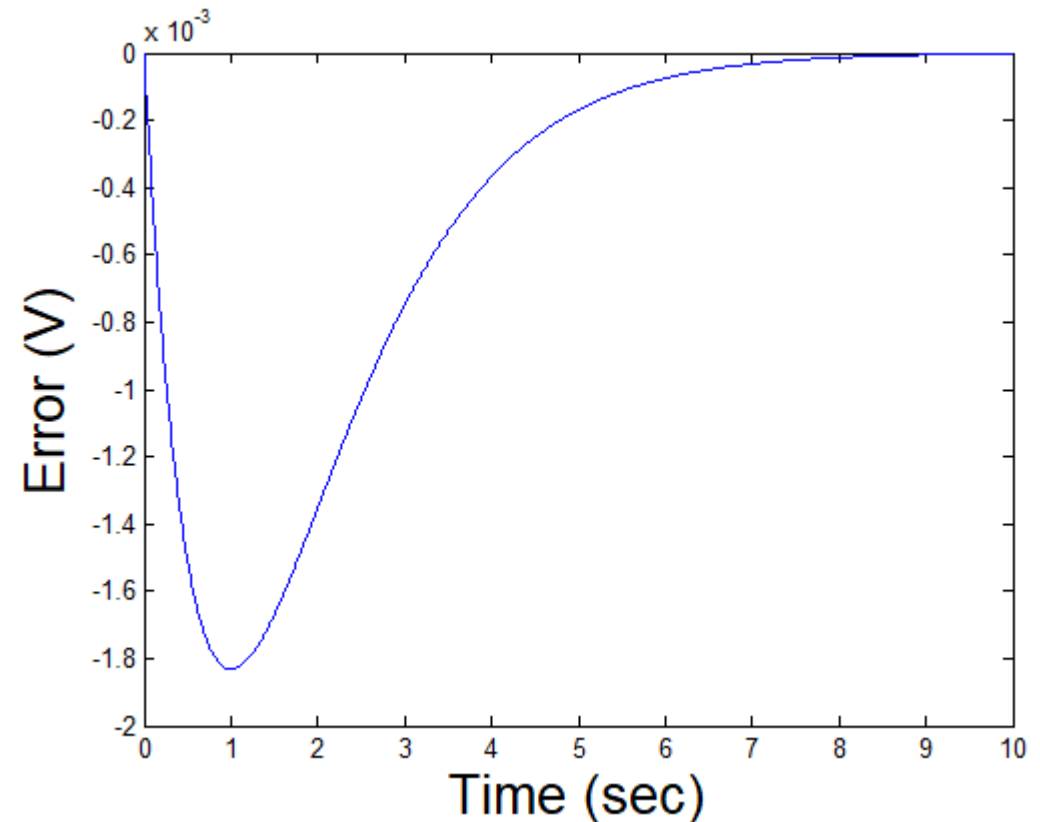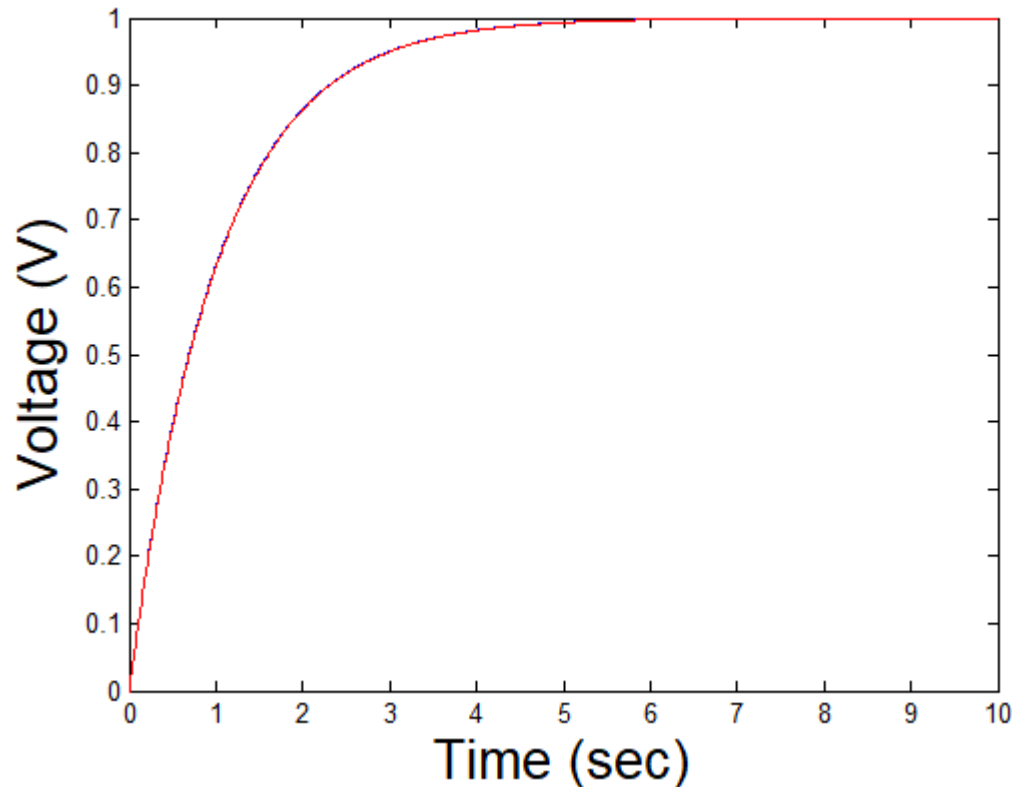
# Case study) $\Delta t = 0.01$

- Ten times shorter time spacing, again
  - The difference becomes almost invisible.
  - Still, we have the maximum difference larger than 0.01 V.



# Another method

- Gear's 2<sup>nd</sup> order method
  - Assume a constant time spacing,  $\Delta t$ .
  - Then, for  $i \geq 2$ ,

$$\left. \frac{\partial f}{\partial t} \right|_{t_i} \approx \frac{1.5f(t_i) - 2f(t_{i-1}) + 0.5f(t_{i-2})}{\Delta t}$$

- For  $i = 1$ , just use the backward Euler method.
- It means that

$$\frac{V_X(t_i) - V_{in}(t_i)}{R} + C \frac{1.5V_X(t_i) - 2V_X(t_{i-1}) + 0.5V_X(t_{i-2})}{\Delta t} = 0$$

# After re-arranging terms,



- A slightly different expression for  $V_X(t_i)$ 
  - Compare it against the backward Euler:

$$(1.5 + \Delta t)V_X(t_i) = 2V_X(t_{i-1}) - 0.5V_X(t_{i-2}) + \Delta t$$

$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t$$

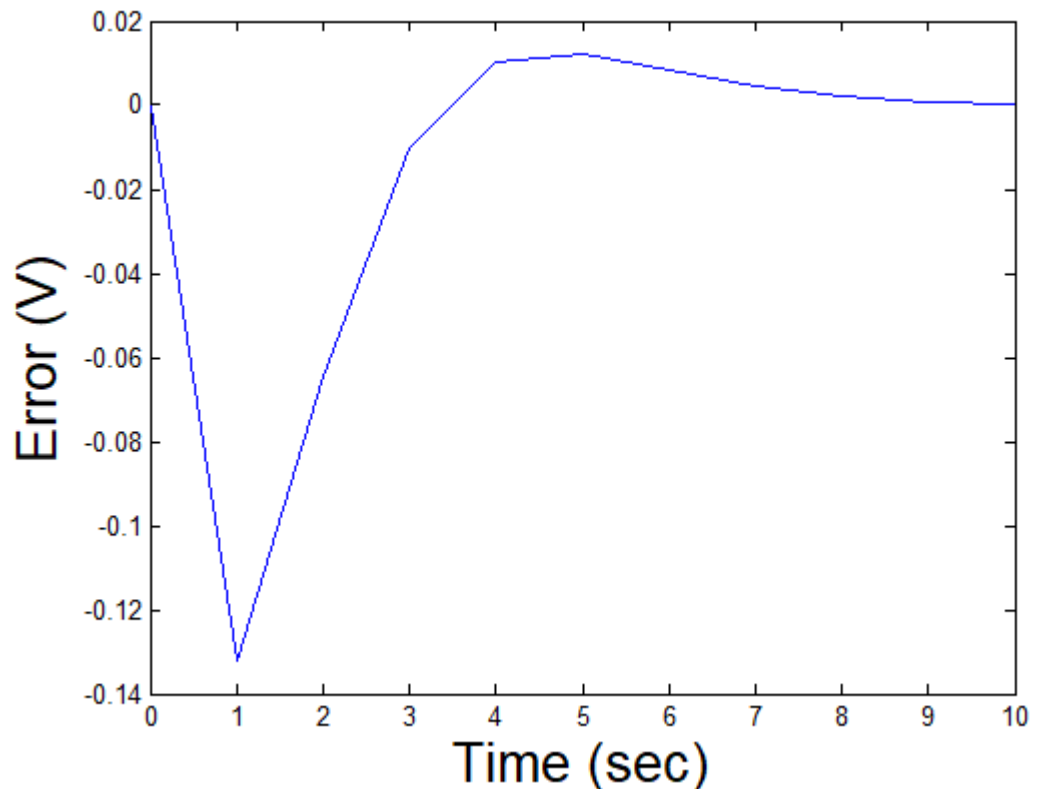
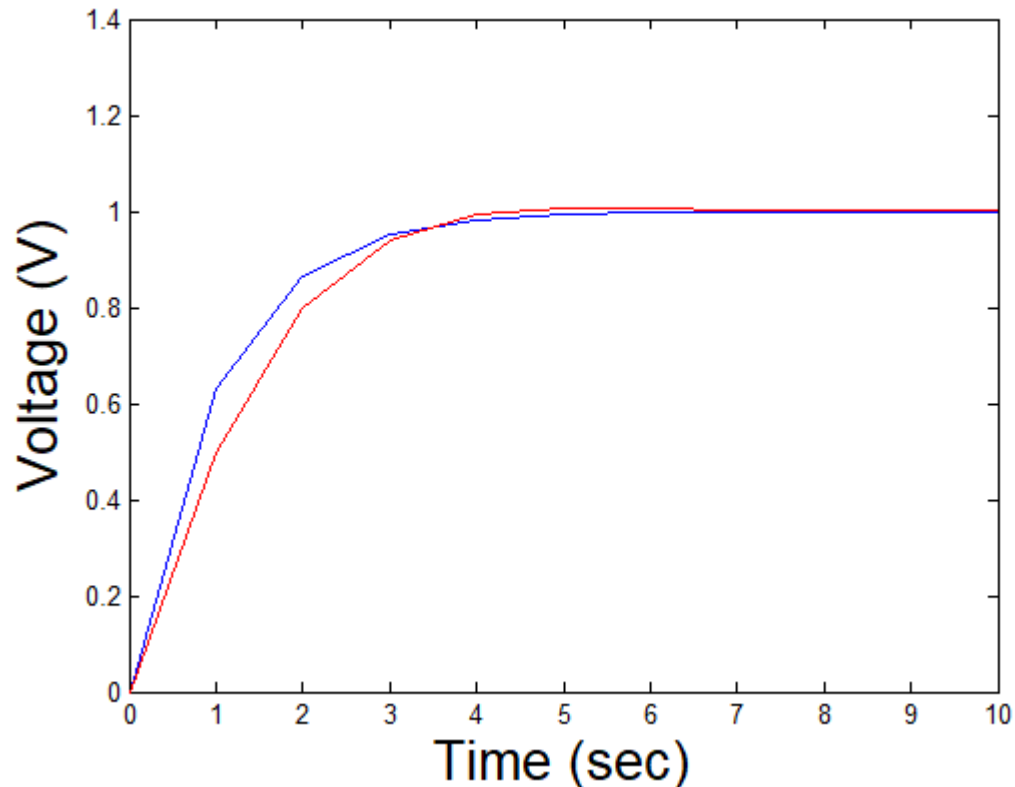
# Case study) $\Delta t = 1$ with Gear's method

- Run the simulation up to 10 sec, again.
  - The maximum error is determined by the first backward Euler step.



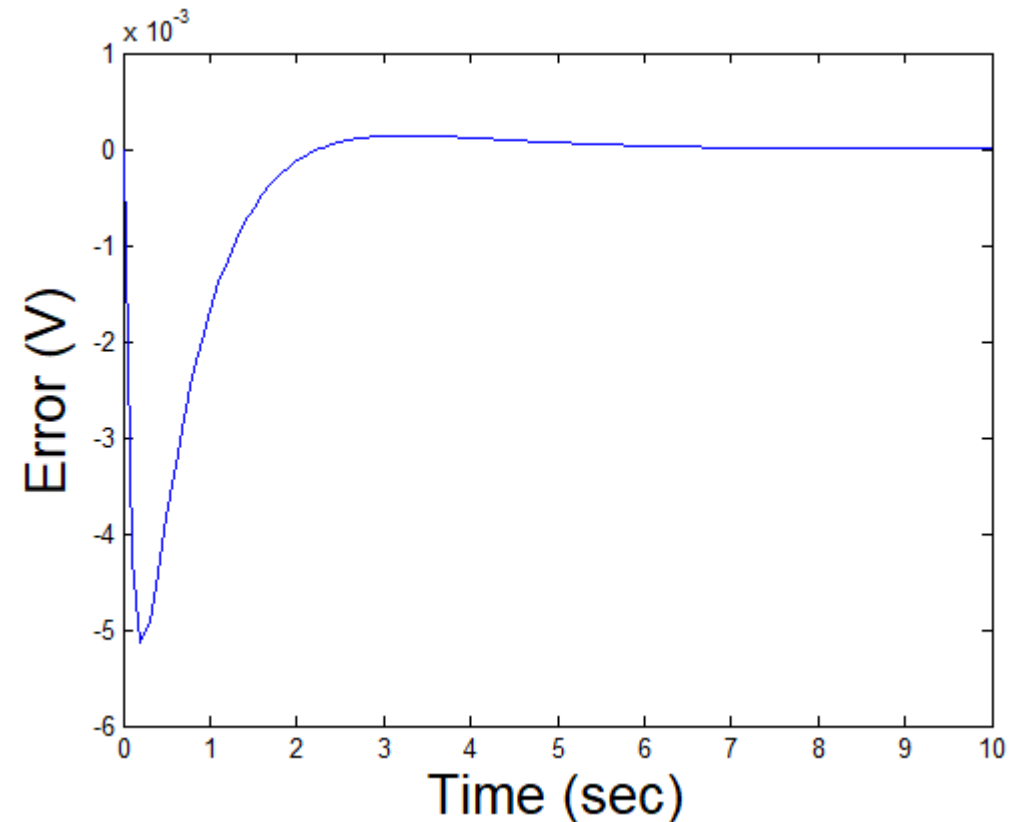
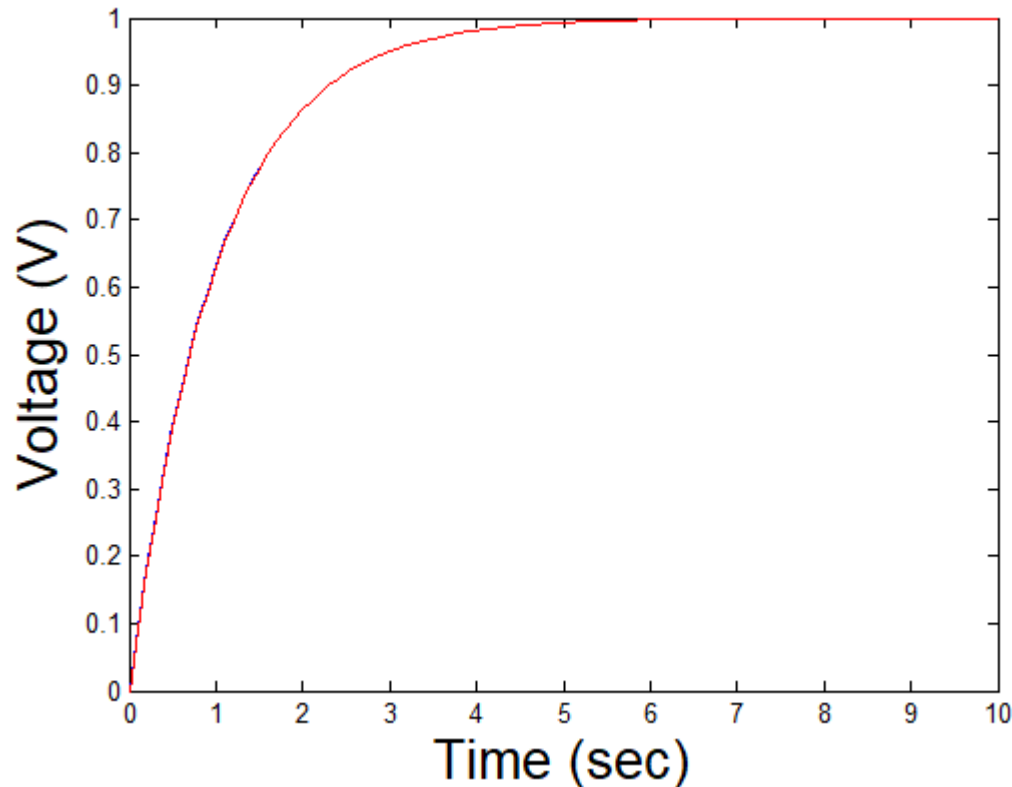
# Case study) $\Delta t = 0.1$ with Gear's method

- Ten times shorter time spacing
  - The difference becomes almost invisible.
  - The maximum difference is smaller than that of the backward Euler.


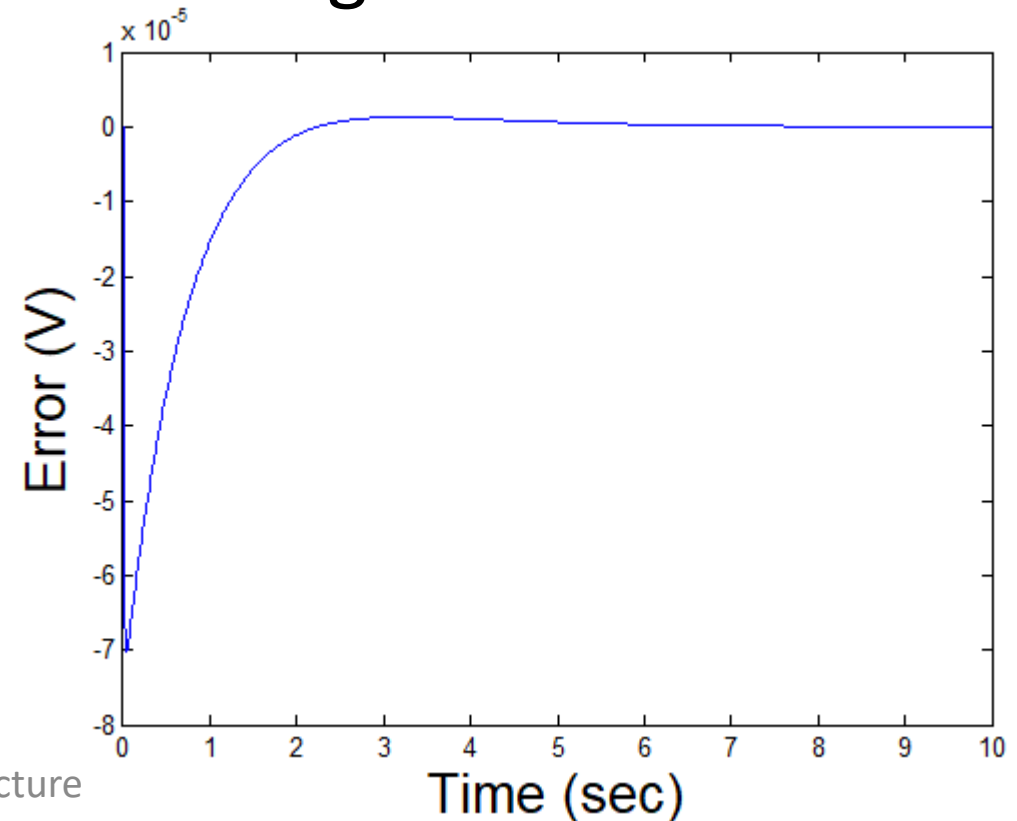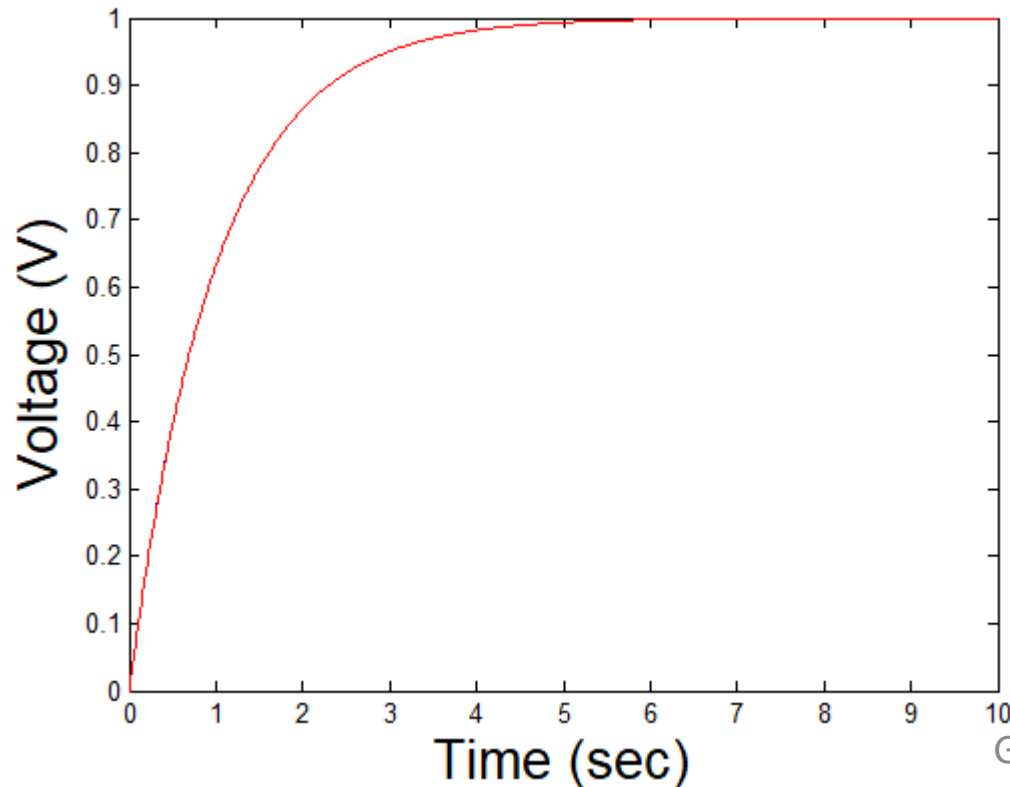
# Case study) $\Delta t = 0.01$

- Ten times shorter time spacing, again
  - Much smaller difference is obtained.
- In summary, the error is rapidly decreasing with a smaller  $\Delta t$ .





# Sinusoidal voltage source



- Apply a sine wave with its amplitude of 1 V.
  - The frequency is 1 Hz.
  - Then, the amplitude of  $V_X$  should be  $\frac{1}{\sqrt{1+(2\pi)^2}}$  V. (0.15718 V)
  - Investigate the amplitude with various  $\Delta t$  values.

$$(1.5 + \Delta t)V_X(t_i) = 2V_X(t_{i-1}) - 0.5V_X(t_{i-2}) + \Delta t \sin 2\pi t$$

$$(1 + \Delta t)V_X(t_i) = V_X(t_{i-1}) + \Delta t \sin 2\pi t$$
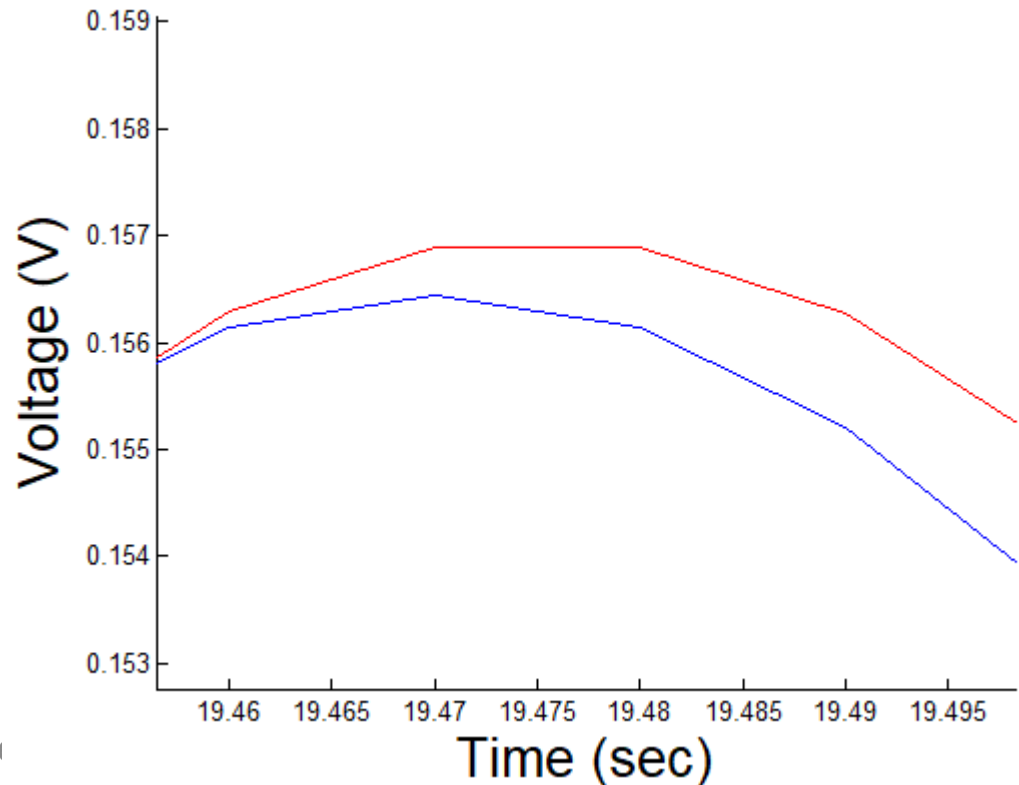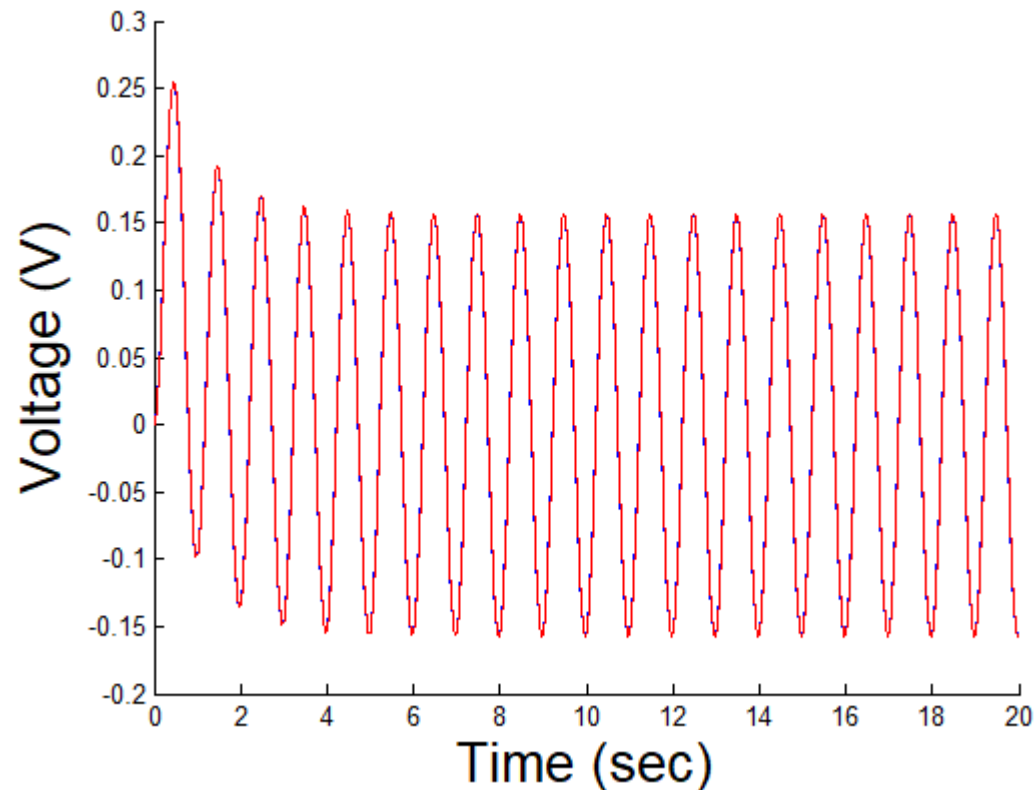
# Case study) $\Delta t = 0.01$

- Only ten points in a period
  - 20 cycles are passed. (Sufficiently stabilized)
  - Gear's method predicts a larger amplitude, close to 0.15718 V.



# Thank you!